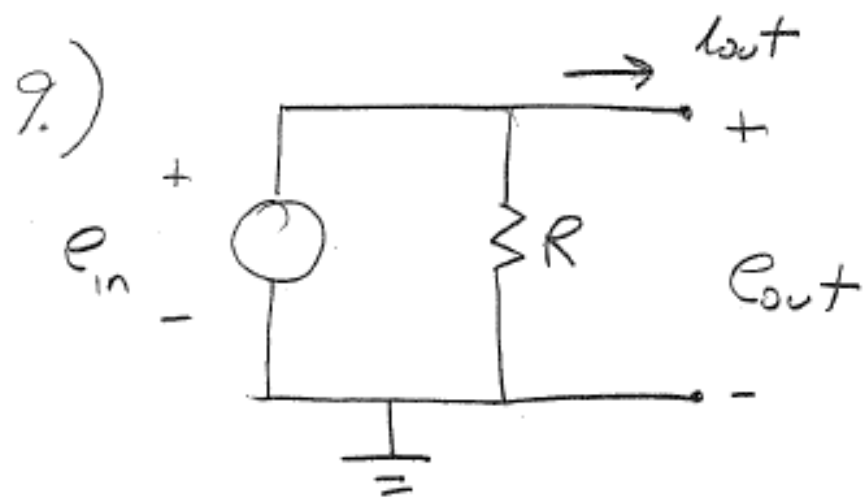


Problem Set # 2


1

- 1.) What is the resistance of a kilometer-long piece of 14-gage copper wire?
($d_{\text{wire}} = 0.06408$ inches).
- 2.) Determine the possible range of resistance values for:
 - (a) R_1 red-brown-yellow-gold
 - (b) R_2 black-violet-orange-gold
 - (c) Series combination of R_1 and R_2
 - (d) Parallel combination of R_1 and R_2
- 3.) When using a potentiometer as a "trim pot", it is usually placed in series with another fixed-value resistor. Why is it not placed in parallel?

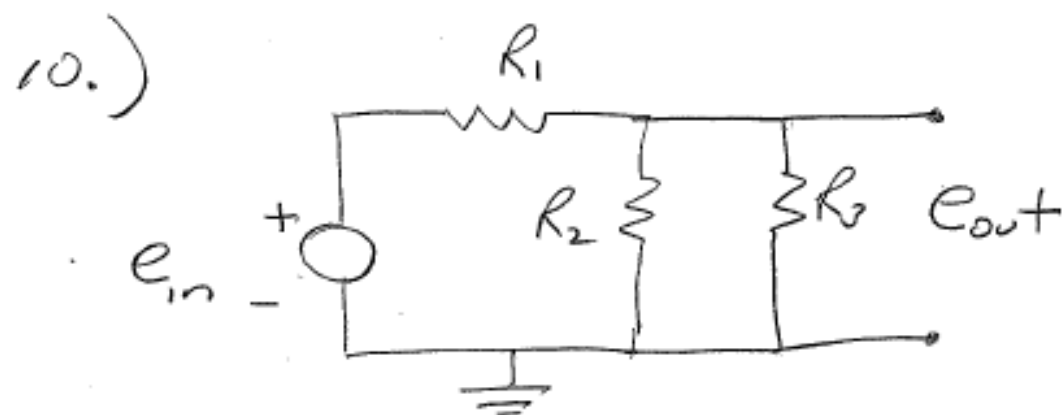- 4.) Does it matter in which direction you assume current flows when applying Kirchhoff's laws to a circuit? Why?
- 5.) You quickly need a $50\ \Omega$ resistor but have a supply of only $100\ \Omega$ resistors. What can you do?
- 6.) Using Ohm's Law, KVL, and KCL derive an expression for the equivalent resistance of three parallel resistors R_1 , R_2 , and R_3 .
- 7.) Derive current-division formulae for three resistors in parallel.
- 8.) Given two resistors R_1 and R_2 , where $R_1 \gg R_2$, prove that the parallel combination is $\approx R_2$.



Assuming $i_{out} = 0$,
plot e_{out} vs. R
as R varies
from 1Ω to $1k\Omega$
in 1Ω increments.




$R_1 = 1k\Omega$
 $R_2 = 2k\Omega$
 $R_3 = 3k\Omega$
 $e_{in} = 5V$

- (a) Find i_{R_1}
- (b) Find i_{R_3}
- (c) Find e_{R_2}

11.) Consider the circuit shown.

4

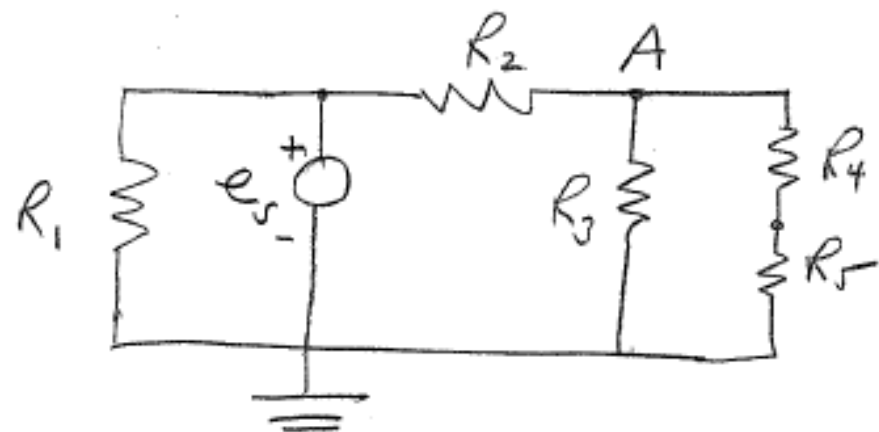


$$\begin{aligned} R_1 &= 1 \text{ k}\Omega \\ R_2 &= 2 \text{ k}\Omega \\ R_3 &= 3 \text{ k}\Omega \\ R_4 &= 4 \text{ k}\Omega \\ R_5 &= 1 \text{ k}\Omega \\ e_s &= 10 \text{ V} \end{aligned}$$

Determine:

- total equivalent resistance seen by e_s .
- voltage at node A
- current through R_3

12.) Find the equivalent resistance of the circuit below as seen by the voltage source.

5

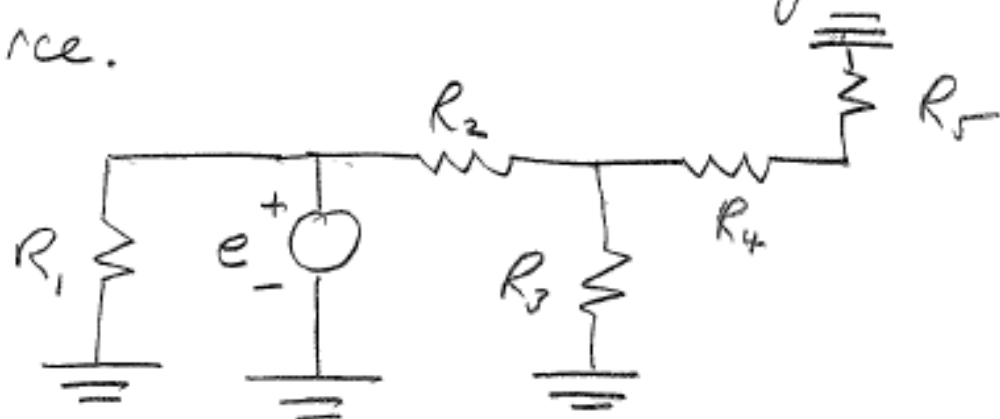

$$\begin{aligned} R_1 &= 1 \text{ k}\Omega \\ R_2 &= 2 \text{ k}\Omega \\ R_3 &= 3 \text{ k}\Omega \\ R_4 &= 4 \text{ k}\Omega \\ R_5 &= 5 \text{ k}\Omega \end{aligned}$$